HOME TASK

Aim : The LED should turn on and off by alternating button presses

Circuit diagram:

